# **Introduction to Computing System**

# Homework 2 Answer

Due date: 00:00 on July 8, 2018

Yale N. Patt Jingwen Leng Summer 2018

## **Homework**

#### 3.4

wire

wire

no wire no wire

#### 3.6


A B C Ζ D 0 0 1 1 0 1 0 0 1 0 1 0 0 1 0 1 1 0 0 1

Z = A AND B

#### 3.14

14

3.16

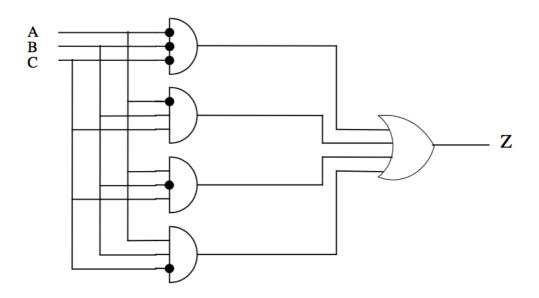

#### 3.24

a X = 0, S = A + B; X = 1, S = A + C

b Figure 3-39 with the following two modifications:

(1) C = NOT(B) (2) Carry-in = X

#### 3.25

- a. 3
- b. 3
- c. 3\*4=12
- d. 3\*32 = 96

#### 3.28

- a. 3
- b. 3
- c. 9
- d. 4

e.

## A[1]A[0]B[1]B[0]Y

- 0 0 0 0 0000
- 0 0 0 1 0000
- 0 0 1 0 0000
- 0 0 1 1 0000
- 0 1 0 0 0000
- 0 1 0 1 0001
- 0 1 1 0 0010
- 0 1 1 1 0011
- 1 0 0 0 0000
- 1 0 0 1 0010
- 1 0 1 0 0100

- 1 0 1 1 0110
- 1 1 0 0 0000
- 1 1 0 1 0011
- 1 1 1 0 0110
- 1 1 1 1 1001

f.

It is easy and omitted.

## 3.29

Nope.

#### 3.33

- a. 11 0
- b. 6 3
- c.  $2^6 6 = 4$

## 3.34

- a. 4
- b. 4
- c. 0001


#### 3.35

2^ 22 \* 3 = 12582912

## 3.36

Nope.

## 3.41

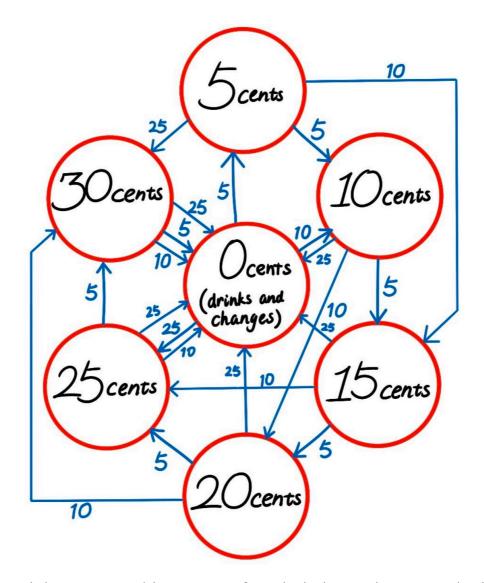

(The graph here is created by Cao Siyu, for it looks better than mine. Thank Cao Siyu!)